

Electric Circuits Worksheet

1. What are the potential differences, V_1 and V_2 , in the circuit shown?


V_1 in parallel w/ 2.0V & 3.0V

$$V_1 = 5.0V$$

V_1 (in series w/ V_2)

$$6.0 = V_1 + V_2$$

$$V_2 = 1.0V$$

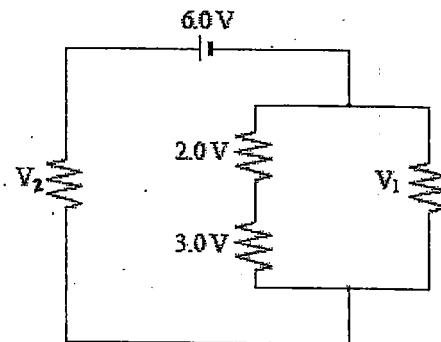

2. The total resistance between points X and Y is 14.0 Ω. What is the value of R?

$$R_T = 14.0 \Omega$$


$$14 = 8.0 + R_{eq}$$

$$R_{eq} = 6.0 \Omega$$

$$\frac{1}{6} = \frac{1}{20} + \frac{1}{60} + \frac{1}{R}$$

$$\left(\frac{1}{6} - \frac{1}{20} - \frac{1}{60} \right)^{-1} = R$$

$$R = 10 \Omega$$

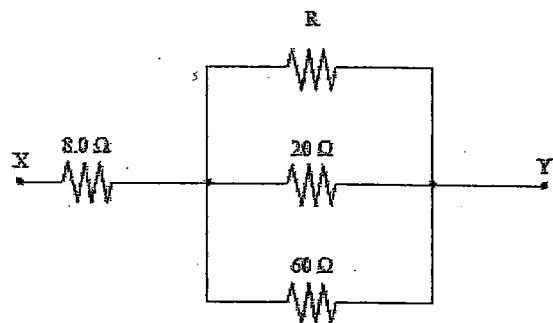

3. A voltmeter is connected across a 3.0 Ω resistor in the circuit shown. What is the reading on the voltmeter?

$$R_T = R_1 + R_2 = \left(\frac{1}{6} + \frac{1}{6} \right)^{-1} = 3.0 \Omega$$

$$R_T = R_3 + R_{eq} = 6.0 \Omega$$


$$I_T = \frac{V_T}{R_T} = \frac{12.0}{6.0} = 2.0A$$

$$I_3 = I_T = 2.0A$$

$$V_3 = I_3 R_3 = (2.0)(3.0)$$

$$V_3 = 6.0V$$

Need I_3 to find

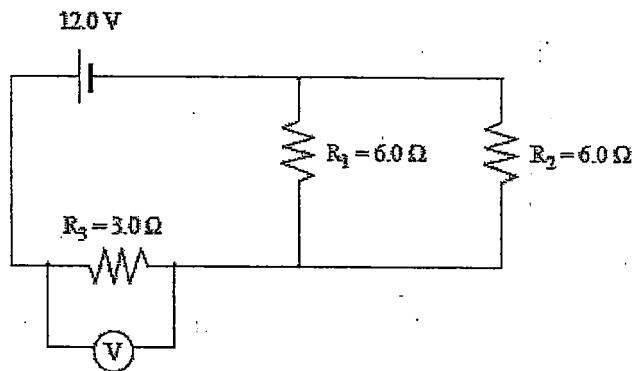

4. Find the current through the battery in the circuit shown.

$$R_{eq}(R_2 \& R_3) = \left(\frac{1}{9} + \frac{1}{18} \right)^{-1} = 6 \Omega$$

$$V_{(2\&3)} = 12 - 3 = 9V$$


$$\text{or } I_2 = \frac{9.0}{9.0} = 1.0A$$

$$I_{2\&3} = I_T = \frac{V_{2\&3}}{R_{2\&3}} = \frac{9}{6} = 1.5A$$

$$I_3 = \frac{9.0}{12.0} = 0.5A$$

$$I_T = 1.5A$$

$$= 1.5V$$

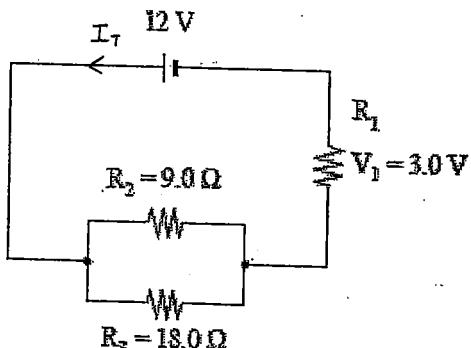


5. Find the current in the 8.0Ω bulb shown.

$$R_{\text{eq}} = \left(\frac{1}{18} + \frac{1}{9} + \frac{1}{3} \right)^{-1} = 2 \Omega$$

$$R_T = 2 + 8 = 10 \Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{30}{10} = 3 \text{ A}$$

$$I_4 = I_T = 3 \text{ A}$$

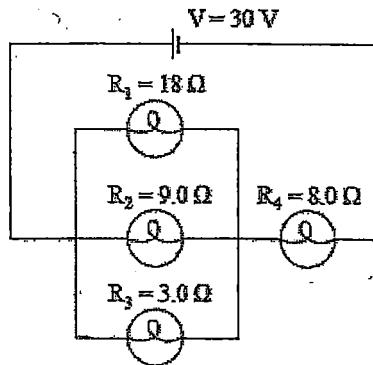

6. The diagram shows part of an electrical circuit.


What is the current through resistor R_1 ?

$$R_{2+3} = \left(\frac{1}{33} + \frac{1}{67} \right)^{-1} = 22.11 \Omega$$

$$R_{\text{eq}}(1,2,3) = \left(\frac{1}{22.11} + \frac{1}{11} \right)^{-1} = 7.35 \Omega$$

$$V_{\text{eq}} = I R = (6.0)(7.35) = 44.1 \text{ V} \quad V_1 = V_{\text{eq}} = 44.1 \text{ V}$$
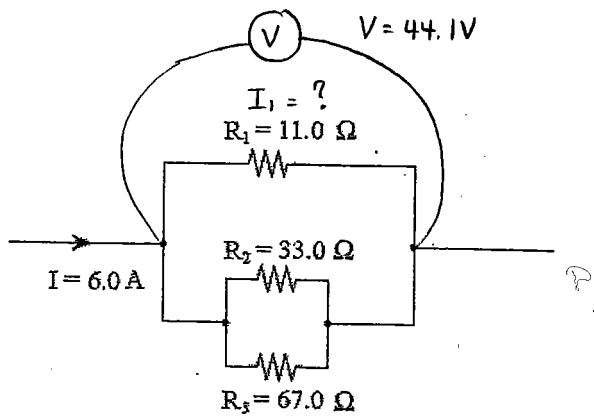
$$I_1 = \frac{V_1}{R_1} = \frac{44.1}{11} = 4 \text{ A}$$



7. What is the voltage, V , of the power supply shown in the circuit?

$$\begin{aligned} V_1 &= I_1 R_1 = (2.0)(12) = 24 \text{ V} \\ V_2 &= 24 \text{ V} \end{aligned} \quad \left. \begin{array}{l} \text{same, in parallel} \\ \text{ } \end{array} \right\}$$

$$I_1 = 2.0 \text{ A}$$

$$V_3 = I_3 R_3 = (6.0)(8.0) = 48 \text{ V}$$

$$I_2 = \frac{V_2}{R_2} = \frac{24}{6} = 4.0 \text{ A}$$


$$V_T = 24 + 48 = 72 \text{ V}$$

$$I_3 = I_T = I_1 + I_2$$

$$\text{or } R_T = 8 + \left(\frac{1}{12} + \frac{1}{6} \right)^{-1}$$

$$= 2.0 + 4.0 = 6.0 \text{ A}$$

$$= 8 + 4 = 12 \Omega$$

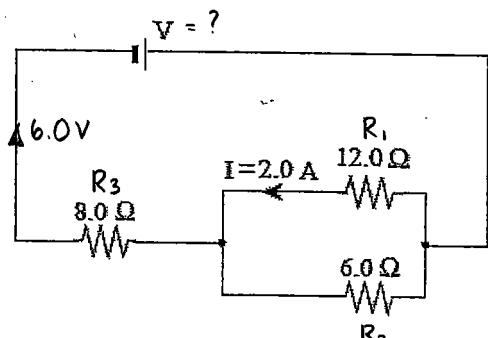

$$\begin{aligned} V_T &= I_T R_T \\ &= (6.0)(12) \\ &= 72 \text{ V} \end{aligned}$$

8. What is the current through the 7.0Ω resistor? How much charge flows through the 7.0Ω resistor in a 30 second interval?


$$R_T = 5 + \left(\frac{1}{10} + \frac{1}{7+10} \right)^{-1}$$

$$I_T = \frac{V_T}{R_T} = \frac{6.0}{11.296}$$

$$= 5 + \left(\frac{1}{10} + \frac{1}{17} \right)^{-1}$$

$$= 0.531 \text{ A}$$

$$= 5 + 6.296$$

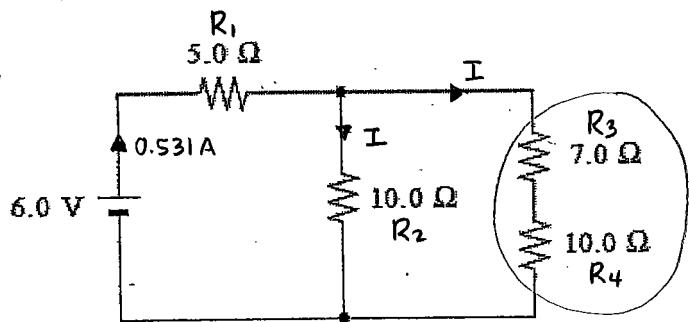

$$V_1 = (0.531)(5) = 2.655 \text{ V}$$

$$V_2 = V_{3+4}$$

$$\begin{aligned} V_2 &= 6.0 - 2.655 \\ &= 3.345 \text{ V} \end{aligned}$$

$$I_3 = \frac{V_{3+4}}{R_{3+4}} = \frac{3.345}{7+10} = 0.197 \text{ A}$$

$$\text{or } I_2 = \frac{3.345}{10} = 0.335 \text{ A}$$

$$\begin{aligned} I_T &- I_2 \\ I_3 &= 0.531 - 0.335 = 0.196 \text{ A} \end{aligned}$$

9. What is the power dissipated in the $9.0\ \Omega$ resistor in the following circuit?


$$R_T = 14 + \left(\frac{1}{9.0} + \frac{1}{18} \right)^{-1} = 14 + 6 = 20\ \Omega$$

$$I_T = \frac{36}{20} = 1.8\ A$$

$$V_1 = I_1 R_1 = (1.8)(14) = 25.2\ V$$

$$V_2 = V_3 = \frac{V_T - V_1}{2} = \frac{36 - 25.2}{2} = 10.8\ V$$

$$I_3 = \frac{10.8}{9} = 1.2\ A$$

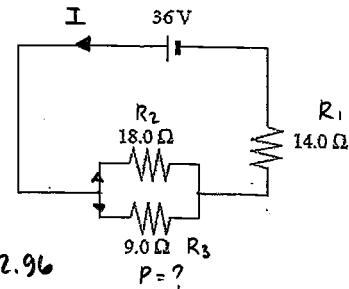

$$\rightarrow P = IV = (1.8)(10.8) = 12.96$$

$$P = 13\ W$$


10. In the following circuit, what is the power dissipated by resistor R_1 ?

$$V_2 = V_3 = \frac{V_T - V_1}{2} = \frac{25 - 10}{2} = 15\ V$$

$$I_2 = \frac{15}{15} = 1\ A$$

$$I_3 = \frac{15}{10} = 1.5\ A$$
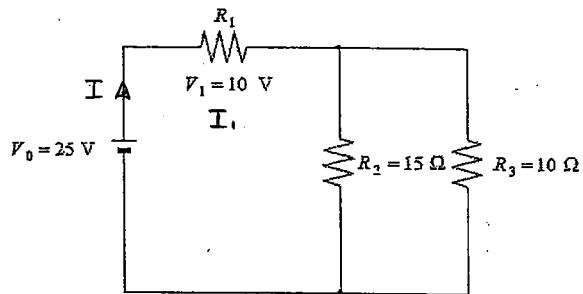
$$I_1 = I_T = I_2 + I_3 = 1 + 1.5 = 2.5\ A$$



$$P_1 = I_1 V_1 = (2.5)(10) = 25\ W$$

